

EE100B Lab Report #6: Design of Active Bandpass Filters

Fernando Rosales

862086644

Section 21

Abstract

The goal of this lab is to familiarize ourselves with the design of Active Bandpass Filters. We will do this by designing and recording data from a bandpass filter.

Procedure

Begin by calculating Am using formulas : $A_m = g/(9-2g)$

$Q = 3/(9-2G)$ and then calculate the rest of the unknown values needed for the circuit with the

$$H(s) = \frac{RC \left(1 + \frac{R_5}{R_4} \right) s}{R^2 C^2 s^2 + RC \left(7 - 2 \frac{R_5}{R_4} \right) s + 9}$$

following formulas. $G = 1 + R_5/R_4$ $F_c = 1/2\pi RC$

From here use MATLAB to create a plot of the magnitude and phase response using the information found. From here construct the circuit using the calculated information and run a simulation with a sine (0 10 5) to start filling out the table. Change the value of the 10 according to the table frequencies to fill out the rest of the table. From here create a plot based off the table values.

Analysis

$$A_m = g/(9-2g)$$

$$Q = 3/(9-2G)$$

$$G = 3$$

$$A_m = 1$$



$$G = 1 + R_5/R_4$$

$$R_4 = 500$$



$$F_c = 1/2\pi RC$$

$$R = 4.77k$$

$$H(s) = .33$$

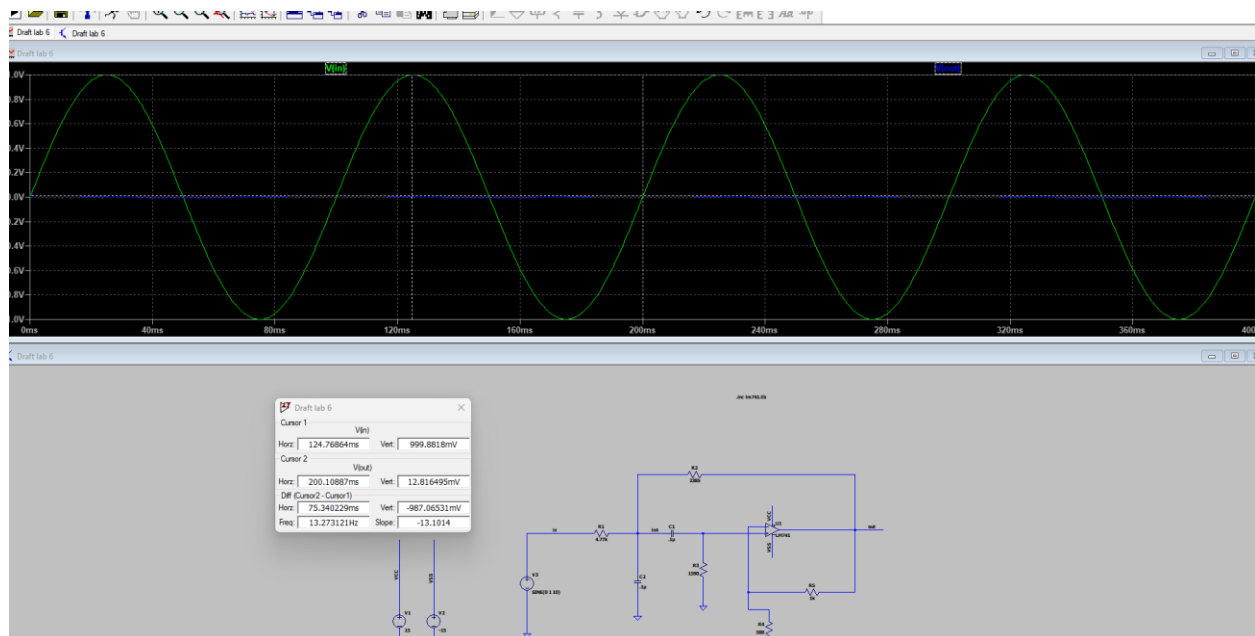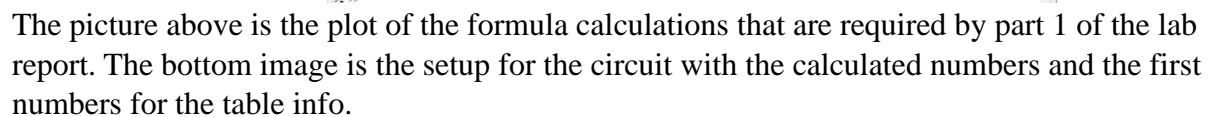

[illegible]

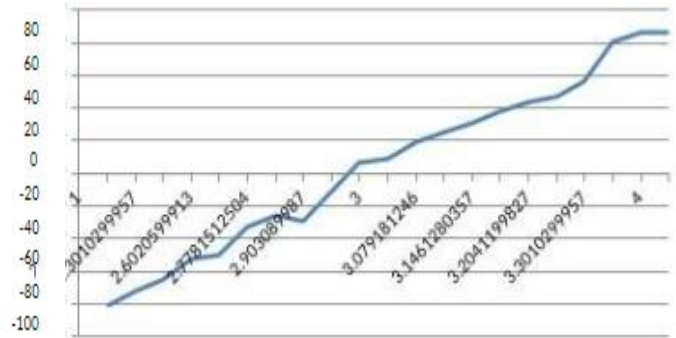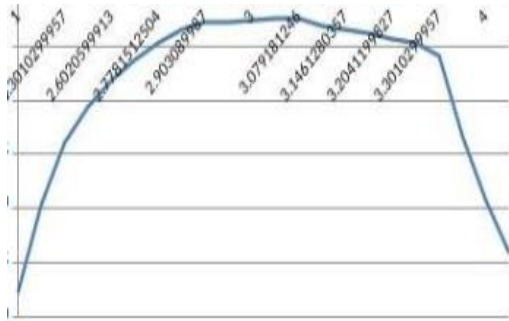

These 2 pictures are the gain and phase graphs required at the end of the lab based off the table entries. This is using excel instead of MATLAB since MATLAB is not my strong suit.

Problems

A couple of issues occurred during the lab. One issue is when I tried to put in the opAmp. The method of .inc opamp.lib was not working so I decided to find it online however im not sure if I got the right one, this might have lead to some inaccuracies in the values. The second issue is the plots on excel might not be accurate because although I know excel better than MATLAB I still am not proficient, Other than that the I am confident in the data.

Conclusion

The lab was successful in getting us familiar with designing Active Bandpass filters. There were a couple of hiccups with the setup but overall the goal was met. The lab was again not difficult to follow and easy to complete.